

# Basic Processing Unit & Pipelining

## MODULE 5: BASIC PROCESSING UNIT

### SOME FUNDAMENTAL CONCEPTS

The processing unit which executes machine instructions and coordinates the activities of other units of computer is called the Instruction Set Processor (ISP) or processor or Central Processing Unit (CPU).

The primary function of a processor is to execute the instructions stored in memory. Instructions are fetched from successive memory locations and executed in processor, until a branch instruction occurs.

- To execute an instruction, processor has to perform following 3 steps:
  1. Fetch contents of memory-location pointed to by PC. Content of this location is an instruction to be executed. The instructions are loaded into IR,  
Symbolically, this operation is written as:  
 $IR \leftarrow [PC]$
  2. Increment PC by 4.  
 $PC \leftarrow [PC] + 4$
  3. Carry out the actions specified by instruction (in the IR).

The steps 1 and 2 are referred to as **Fetch Phase**.

Step 3 is referred to as **Execution Phase**.

- The operation specified by an instruction can be carried out by performing one or more of the following actions:
  - 1) Read the contents of a given memory-location and load them into a register.
  - 2) Read data from registers or memory location.
  - 3) Perform an arithmetic or logic operation and place the result into a register.
  - 4) Store data from a register into a given memory-location.
- The hardware-components needed to perform these actions are shown in Figure 5.1.

# Basic Processing Unit & Pipelining

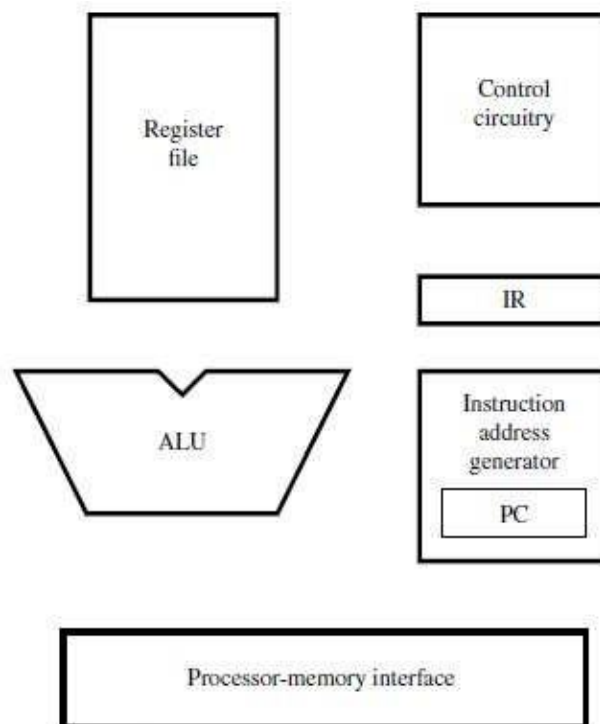


Figure 5.1 Main hardware components of a processor.

## SINGLE BUS ORGANIZATION

- Here the processor contains only a single bus for the movement of data, address and instructions.
- ALU and all the registers are interconnected via a **Single Common Bus** (Figure 7.1).
- Data & address lines of the external **memory-bus** is connected to the internal processor-bus via MDR & MAR respectively.

(MDR -> Memory Data Register, MAR -> Memory Address Register).

- **MDR** has 2 inputs and 2 outputs. Data may be loaded
  - into MDR either from memory-bus (external) or
  - from processor-bus (internal).
- **MAR**'s input is connected to internal-bus; MAR's output is connected to external-bus. (address sent from processor to memory only)
- **Instruction Decoder & Control Unit** is responsible for
  - Decoding the instruction and issuing the control-signals to all the units inside the processor.
  - implementing the actions specified by the instruction (loaded in the IR).
- **Processor Registers** - Register R0 through R(n-1) are also called as General Purpose Register.

The programmer can access these registers for general-purpose use.

## Basic Processing Unit & Pipelining

- **Temporary Registers** – There are 3 temporary registers in the processor. Registers - **Y**, **Z** & **Temp** are used for temporary storage during program-execution. The programmer cannot access these 3 registers.
- In **ALU**, 1) “A” input gets the operand from the output of the multiplexer (MUX).  
2) “B” input gets the operand directly from the processor-bus.
- There are 2 options provided for “A” input of the ALU.
- MUX is used to select one of the 2 inputs.
- **MUX** selects either  
→ output of Y or  
→ constant-value 4( which is used to increment PC content).

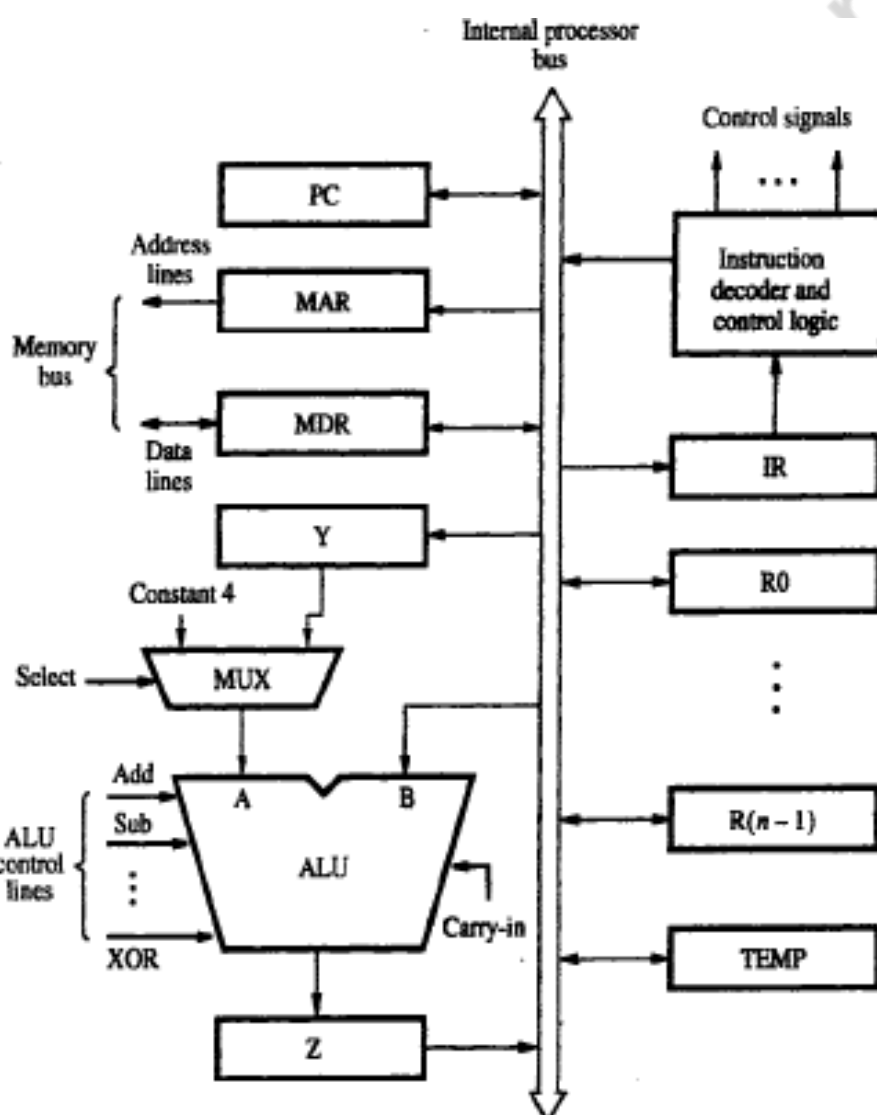


Figure 7.1 Single-bus organization of the datapath inside a processor.

- An instruction is executed by performing one or more of the following operations:
  - 1) Transfer a word of data from one register to another or to the ALU.
  - 2) Perform arithmetic or a logic operation and store the result in a register.

## Basic Processing Unit & Pipelining

---

- 3) Fetch the contents of a given memory-location and load them into a register.
- 4) Store a word of data from a register into a given memory-location.
  - **Disadvantage:** Only one data-word can be transferred over the bus in a clock cycle.
  - Solution:** Provide multiple internal-paths. Multiple paths allow several data-transfers to take place in parallel.

## Basic Processing Unit & Pipelining

---

### REGISTER TRANSFERS

- Instruction execution involves a sequence of steps in which data are transferred from one register to another.
- For each register, two control-signals are used: Riin & Riout. These are called **Gating Signals**.
- Riin=1 □ data on bus is loaded into Ri. Riout=1 □ content of Ri is placed on bus.
- Riout=0, □ bus can be used for transferring data from other registers.
- For example, *Move R1, R2*; This transfers the contents of register R1 to register R2. This can be accomplished as follows:
  - 1) Enable the output of registers R1 by setting R1out to 1 (Figure 7.2). This places the contents of R1 on processor-bus.
  - 2) Enable the input of register R2 by setting R2out to 1. This loads data from processor-bus into register R4.
- All operations and data transfers within the processor take place within time-periods defined by the **processor-clock**.

## Basic Processing Unit & Pipelining

- The control-signals that govern a particular transfer are asserted at the start of the

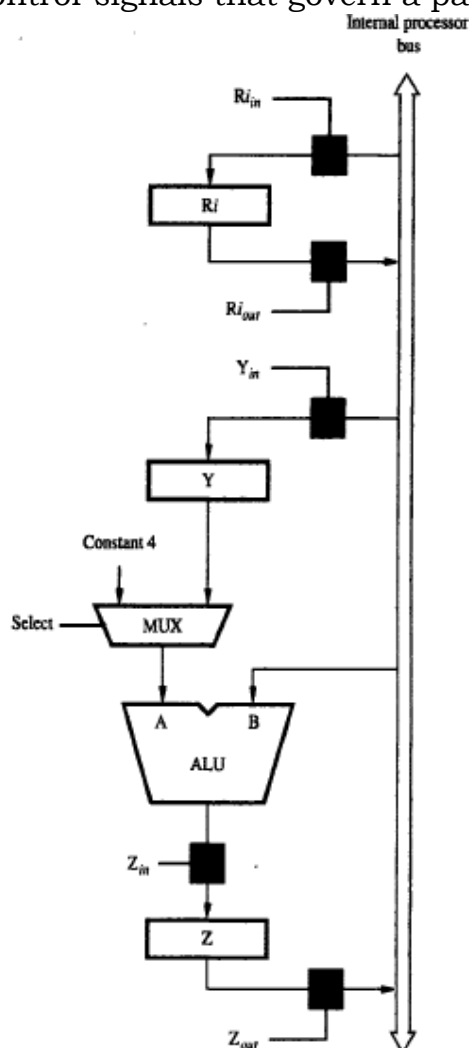


Figure 7.2 Input and output gating for the registers in Figure 7.1.

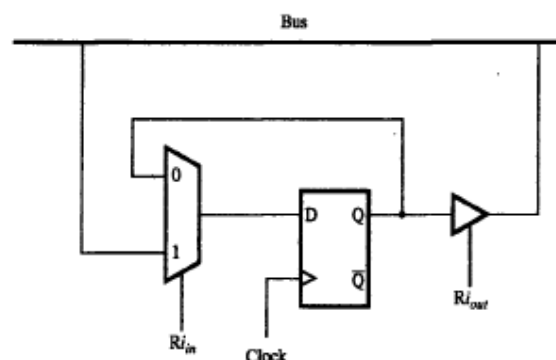


Figure 7.3 Input and output gating for one register bit.

clock cycle.

### Input & Output Gating for one Register Bit

- A 2-input multiplexer is used to select the data applied to the input of an edge-triggered D flip-flop.
- $Ri_{in}=1$   $\square$  mux selects data on bus. This data will be loaded into flip-flop at rising-edge of clock.  $Ri_{in}=0$   $\square$  mux feeds back the value currently stored in flip-flop (Figure 7.3).
- Q output of flip-flop is connected to bus via a tri-state gate.  $Ri_{out}=0$   $\square$  gate's output is in the high-impedance state.
- $Ri_{out}=1$   $\square$  the gate drives the bus to 0 or 1, depending on the value of Q.

## Basic Processing Unit & Pipelining

---

[www.takeiteasyengineers.com](http://www.takeiteasyengineers.com)

## Basic Processing Unit & Pipelining

### PERFORMING AN ARITHMETIC OR LOGIC OPERATION

- The ALU performs arithmetic operations on the 2 operands applied to its A and B inputs.

- One of the operands is output of MUX;

And, the other operand is obtained directly from processor-bus.

- The result (produced by the ALU) is stored temporarily in register Z.

- The sequence of operations for  $[R3] \leftarrow [R1] + [R2]$  is as follows:

1) R1out, Yin

2) R2out, SelectY, Add, Zin

3) Zout, R3in

- Instruction execution proceeds as follows:

Step 1 --> Contents from register R1 are loaded into register Y.

Step 2 --> Contents from Y and from register R2 are applied to the A and B inputs of ALU;

Addition is performed &

Result is stored in the Z register.

Step 3 --> The contents of Z register is stored in the R3 register.

- The signals are activated for the duration of the clock cycle corresponding to that step. All other signals are inactive.

### CONTROL-SIGNALS OF MDR

- The MDR register has 4 control-signals (Figure 7.4):

1) MDRin & MDROUT control the connection to the internal processor data bus &

2) MDRinE & MDROUT control the connection to the memory Data bus.

- MAR register has 2 control-signals.

1) MARin controls the connection to the internal processor address bus &

2) MARout controls the connection to the memory address bus.

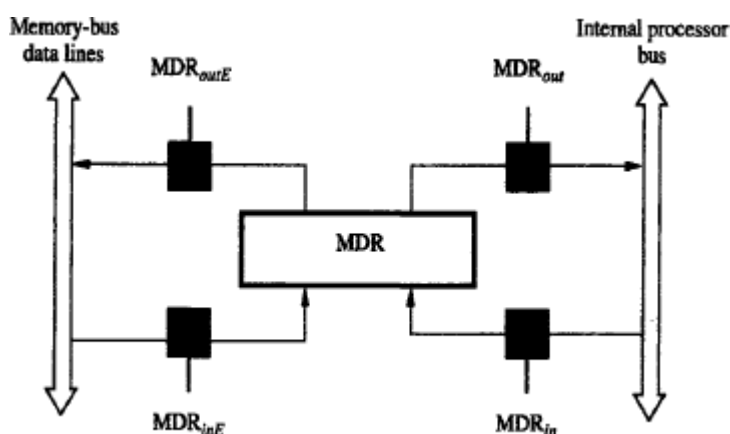


Figure 7.4 Connection and control signals for register MDR.



## Basic Processing Unit & Pipelining

---

### FETCHING A WORD FROM MEMORY

- To fetch instruction/data from memory, processor transfers required address to MAR. At the same time, processor issues Read signal on control-lines of memory-bus.
    - When requested-data are received from memory, they are stored in MDR. From MDR, they are transferred to other registers.
    - The response time of each memory access varies (based on cache miss, memory-mapped I/O). To accommodate this, MFC is used. (MFC  $\square$  Memory Function Completed).
    - MFC is a signal sent from addressed-device to the processor. MFC informs the processor that the requested operation has been completed by addressed-device.
    - Consider the instruction Move (R1),R2. The sequence of steps is (Figure 7.5):
- 1) R1out, MARin, Read ;desired address is loaded into MAR & Read command is issued.
  - 2) MDRinE, WMFC ;load MDR from memory-bus & Wait for MFC response from memory.
  - 3) MDRout, R2in ;load R2 from MDR.
- where WMFC=control-signal that causes processor's control. circuitry to wait for arrival of MFC signal.

## Basic Processing Unit & Pipelining

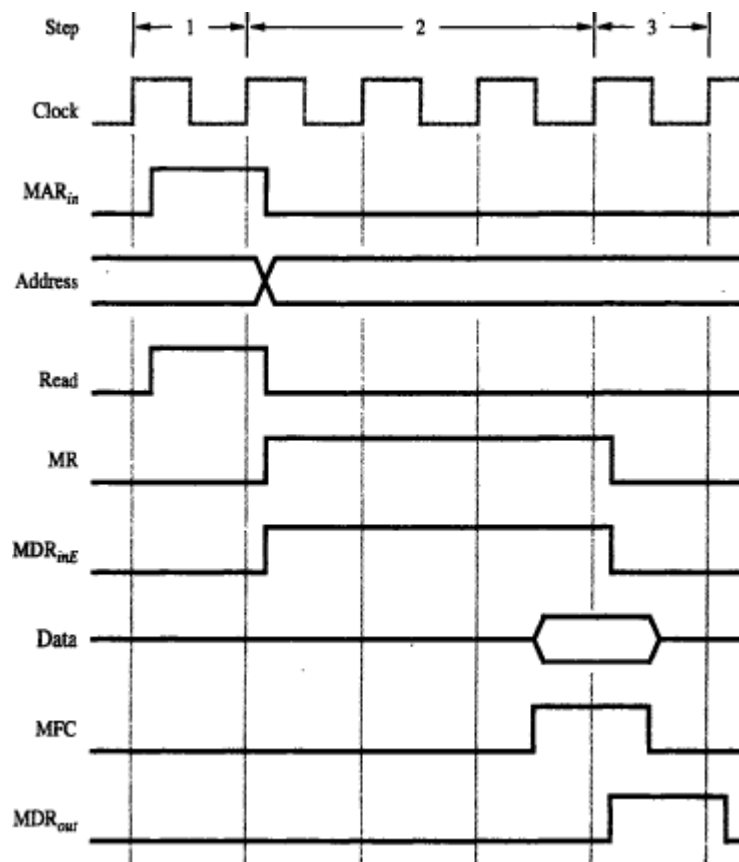


Figure 7.5 Timing of a memory Read operation.

### Storing a Word in Memory

• Consider the instruction *Move R2,(R1)*. This requires the following sequence:

- 1) R1out, MARin ;desired address is loaded into MAR.
- 2) R2out, MDRin, Write ;data to be written are loaded into MDR & Write command is issued.
- 3) MDRoutE, WMFC ;load data into memory-location pointed by R1 from MDR.

## Basic Processing Unit & Pipelining

### EXECUTION OF A COMPLETE INSTRUCTION

• Consider the instruction *Add (R3), R1* which adds the contents of a memory-location pointed by R3 to register R1. Executing this instruction requires the following actions:

- 1) Fetch the instruction.
- 2) Fetch the first operand.
- 3) Perform the addition &
- 4) Load the result into R1.

Step	Action
1	PC <sub>out</sub> , MAR <sub>in</sub> , Read, Select4, Add, Z <sub>in</sub>
2	Z <sub>out</sub> , PC <sub>in</sub> , Y <sub>in</sub> , WMFC
3	MDR <sub>out</sub> , IR <sub>in</sub>
4	R3 <sub>out</sub> , MAR <sub>in</sub> , Read
5	R1 <sub>out</sub> , Y <sub>in</sub> , WMFC
6	MDR <sub>out</sub> , SelectY, Add, Z <sub>in</sub>
7	Z <sub>out</sub> , R1 <sub>in</sub> , End

**Figure 7.6** Control sequence for execution of the instruction *Add (R3), R1*

• Instruction execution proceeds as follows:

Step1--> The instruction-fetch operation is initiated by  
 → loading contents of PC into MAR &  
 → sending a Read request to memory.

The Select signal is set to Select4, which causes the Mux to select constant 4. This value is added to operand at input B (PC's content), and the result is stored in Z.

Step2--> Updated value in Z is moved to PC. This completes the PC increment operation and PC will now point to next instruction.

Step3--> Fetched instruction is moved into MDR and then to IR. The step 1 through 3 constitutes the **Fetch Phase**.

At the beginning of step 4, the instruction decoder interprets the contents of the IR. This enables the control circuitry to activate the control-signals for steps 4 through 7.

The step 4 through 7 constitutes the **Execution Phase**.

Step4--> Contents of R3 are loaded into MAR & a memory read signal is issued.

Step5--> Contents of R1 are transferred to Y to prepare for addition.

Step6--> When Read operation is completed, memory-operand is available in MDR, and the

## Basic Processing Unit & Pipelining

---

addition is performed.

Step7--> Sum is stored in Z, then transferred to R1. The End signal causes a new instruction fetch cycle to begin by returning to step1.

www.takeiteasyengineers.com

## Basic Processing Unit & Pipelining

### BRANCHING INSTRUCTIONS

- Control sequence for an **unconditional branch instruction** is as follows:

Step	Action
1	$PC_{out}, MAR_{in}, Read, Select4, Add, Z_{in}$
2	$Z_{out}, PC_{in}, Y_{in}, WMFC$
3	$MDR_{out}, IR_{in}$
4	$Offset-field-of-IR_{out}, Add, Z_{in}$
5	$Z_{out}, PC_{in}, End$

**Figure 7.7** Control sequence for an unconditional Branch instruction.

- Instruction execution proceeds as follows:
  - Step 1-3--> The processing starts & the fetch phase ends in step3.
  - Step 4--> The offset-value is extracted from IR by instruction-decoding circuit. Since the updated value of PC is already available in register Y, the offset X is gated onto the bus, and an addition operation is performed.
  - Step 5--> the result, which is the branch-address, is loaded into the PC.
- The branch instruction loads the branch target address in PC so that PC will fetch the next instruction from the branch target address.
- The branch target address is usually obtained by adding the offset in the contents of PC.
- The offset X is usually the difference between the branch target-address and the address immediately following the branch instruction.
- In case of **conditional branch**,
  - we have to check the status of the condition-codes before loading a new value into the PC. e.g.:  $Offset-field-of-IR_{out}, Add, Z_{in}, If\ N=0\ then\ End$
  - If  $N=0$ , processor returns to step 1 immediately after step 4. If  $N=1$ , step 5 is performed to load a new value into PC.

## Basic Processing Unit & Pipelining

### MULTIPLE BUS ORGANIZATION

• **Disadvantage of Single-bus organization:** Only one data-word can be transferred over the bus in a clock cycle. This increases the steps required to complete the execution of the instruction

**Solution:** To reduce the number of steps, most processors provide multiple internal-paths. Multiple paths enable several transfers to take place in parallel.

• As shown in fig 7.8, three buses can be used to connect registers and the ALU of the processor.

• All general-purpose registers are grouped into a single block called the **Register File**.

• Register-file has 3 ports:

- 1) Two output-ports allow the contents of 2 different registers to be simultaneously placed on buses A & B.
- 2) Third input-port allows data on bus C to be loaded into a third register during

Step	Action
1	$PC_{out}, R=B, MAR_{in}, Read, IncPC$
2	WMFC
3	$MDR_{outB}, R=B, IR_{in}$
4	$R4_{outA}, R5_{outB}, SelectA, Add, R6_{in}, End$

**Figure 7.9** Control sequence for the instruction Add R4,R5,R6

the same clock-cycle.

- Buses A and B are used to transfer source-operands to A & B inputs of ALU.
- The result is transferred to destination over bus C.
- **Incrementer Unit** is used to increment PC by 4.

• Instruction execution proceeds as follows:

Step 1--> Contents of PC are

→ passed through ALU using  $R=B$  control-signal &

→ loaded into MAR to start memory Read operation. At the same time, PC is incremented by 4.

Step2--> Processor waits for MFC signal from memory.

## Basic Processing Unit & Pipelining

Step3--> Processor loads requested-data into MDR, and then transfers them to IR.

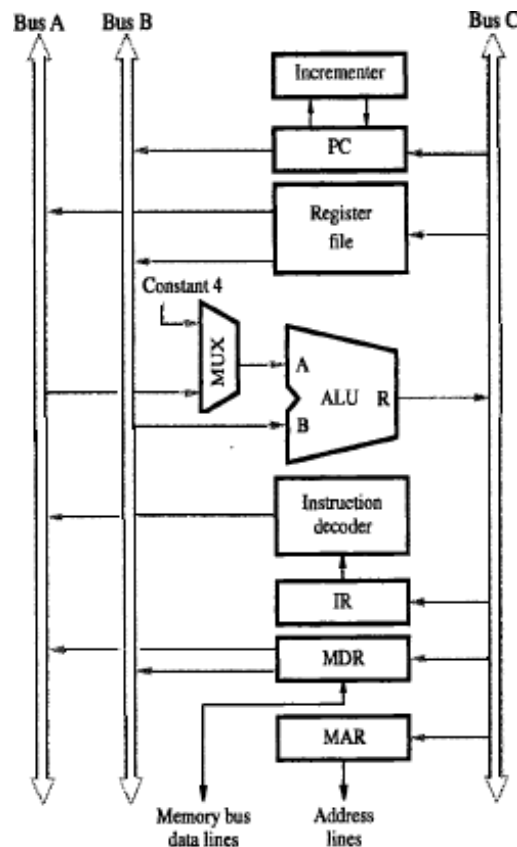


Figure 7.8 Three-bus organization of the datapath.

Step4--> The instruction is decoded and add operation takes place in a single step.

## Basic Processing Unit & Pipelining

---

### COMPLETE PROCESSOR

- This has separate processing-units to deal with integer data and floating-point data.

**Integer Unit** □ → To process integer data. (Figure 7.14).

**Floating Unit** □ → To process floating –point data.

- **Data-Cache** is inserted between these processing-units & main-memory. The integer and floating unit gets data from data cache.
  - **Instruction-Unit** fetches instructions
    - from an instruction-cache or
    - from main-memory when desired instructions are not already in cache.
  - Processor is connected to system-bus & hence to the rest of the computer by means of a **Bus Interface**.
  - Using separate caches for instructions & data is common practice in many processors today.
  - A processor may include several units of each type to increase the potential for concurrent operations.
  - The 80486 processor has 8-kbytes single cache for both instruction and data. Whereas the Pentium processor has two separate 8 kbytes caches for instruction and data.



## Basic Processing Unit & Pipelining

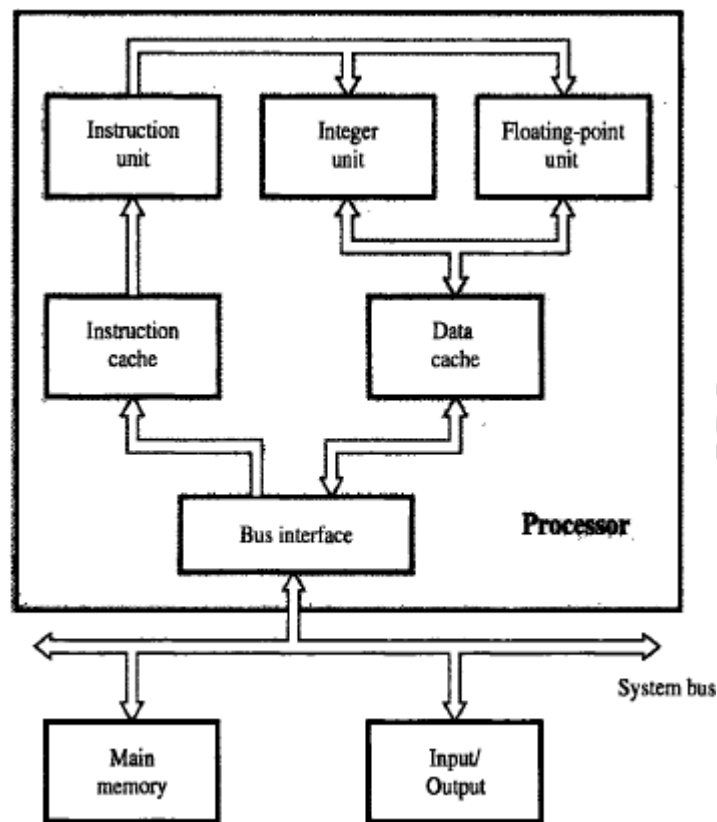


Figure 7.14 Block diagram of a complete processor.

**Note:**

To execute instructions, the processor must have some means of generating the control-signals. There are two approaches for this purpose:

- 1) Hardwired control and 2) Microprogrammed control.

## Basic Processing Unit & Pipelining

### HARDWIRED CONTROL

- Hardwired control is a method of control unit design (Figure 7.11).
- The control-signals are generated by using logic circuits such as gates, flip-flops, decoders etc.
- **Decoder/Encoder Block** is a combinational-circuit that generates required control-outputs depending on state of all its inputs.
- **Instruction Decoder**
  - It decodes the instruction loaded in the IR.
  - If IR is an 8 bit register, then instruction decoder generates  $2^8$ (256 lines); one for each instruction.
  - It consists of a separate output-lines INS1 through INSm for each machine instruction.
  - According to code in the IR, one of the output-lines INS1 through INSm is set to 1, and all other lines are set to 0.
- **Step-Decoder** provides a separate signal line for each step in the control sequence.
- **Encoder**
  - It gets the input from instruction decoder, step decoder, external inputs and condition codes.
  - It uses all these inputs to generate individual control-signals: Yin, PCout, Add, End and so on.
  - For example (Figure 7.12),  $Zin = T1 + T6.ADD + T4.BR$   
;This signal is asserted during time-slot T1 for all instructions.  
during T6 for an Add instruction.  
during T4 for unconditional branch instruction
- When **RUN**=1, counter is incremented by 1 at the end of every clock cycle. When RUN=0, counter stops counting.
  - After execution of each instruction, **end** signal is generated. End signal resets step counter.
  - Sequence of operations carried out by this machine is determined by wiring of logic circuits, hence the name “**hardwired**”.
  - **Advantage:** Can operate at high speed.
  - **Disadvantages:**
    - 1) Since no. of instructions/control-lines is often in hundreds, the complexity of control unit is very high.
    - 2) It is costly and difficult to design.
    - 3) The control unit is inflexible because it is difficult to change the design.

## Basic Processing Unit &amp; Pipelining

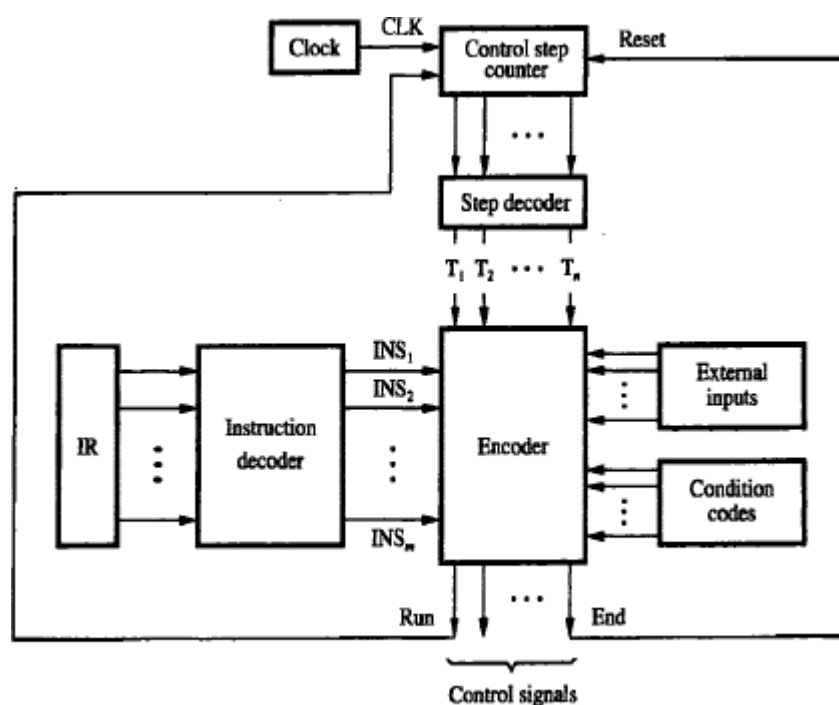


Figure 7.11 Separation of the decoding and encoding functions.

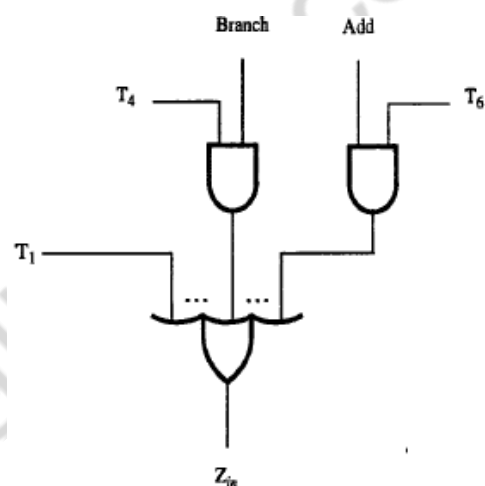


Figure 7.12 Generation of the  $Z_{in}$  control signal

## Basic Processing Unit & Pipelining

### HARDWIRED CONTROL VS MICROPROGRAMMED CONTROL

Attribute	Hardwired Control	Microprogrammed Control
<b>Definition</b>	Hardwired control is a control mechanism to generate control-signals by using gates, flip-flops, decoders, and other digital circuits.	Micro programmed control is a control mechanism to generate control-signals by using a memory called control store (CS), which contains the control- signals.
<b>Speed</b>	Fast	Slow
<b>Control functions</b>	Implemented in hardware.	Implemented in software.
<b>Flexibility</b>	Not flexible to accommodate new system specifications or new instructions.	More flexible, to accommodate new system specification or new instructions redesign is required.
<b>Ability to handle large or complex instruction sets</b>	Difficult.	Easier.
<b>Ability to support operating systems &amp; diagnostic features</b>	Very difficult.	Easy.
<b>Design process</b>	Complicated.	Orderly and systematic.
<b>Applications</b>	Mostly RISC microprocessors.	Mainframes, some microprocessors.
<b>Instruction set size</b>	Usually under 100 instructions.	Usually over 100 instructions.
<b>ROM size</b>	-	2K to 20-40 microinstructions.

## Basic Processing Unit & Pipelining

Chip area efficiency	Uses least area.	Uses more area.
Diagram	<p>This diagram illustrates a basic processing unit that uses the least area. It features a central cloud-shaped component representing the processor. Above the processor is a rectangular box labeled 'State register'. Five upward-pointing arrows, labeled 'Control signals', connect the state register to the processor. A feedback loop is shown with an arrow pointing from the processor back to the state register. To the left of the processor, a vertical line is labeled 'Status information'.</p>	<p>This diagram illustrates a basic processing unit that uses more area. It features a central cloud-shaped component representing the processor. Above the processor is a rectangular box labeled 'Microinstruction register'. Five upward-pointing arrows, labeled 'Control signals', connect the microinstruction register to the processor. Below the processor is a rectangular box labeled 'Control storage'. An arrow points from the control storage up to the microinstruction register. To the right of the control storage is a small rectangular box labeled 'Control storage address register', with an arrow pointing from it to the control storage. A feedback loop is shown with an arrow pointing from the processor back to the control storage. To the left of the processor, a vertical line is labeled 'Status information'.</p>

## Basic Processing Unit & Pipelining

### MICROPROGRAMMED CONTROL

- Microprogramming is a method of control unit design (Figure 7.16).
  - Control-signals are generated by a program similar to machine language programs.
  - **Control Word(CW)** is a word whose individual bits represent various control-signals (like Add, PCin).
  - Each of the control-steps in control sequence of an instruction defines a unique combination of 1s & 0s in CW.
  - Individual control-words in microroutine are referred to as **microinstructions** (Figure 7.15).
  - A sequence of CWs corresponding to control-sequence of a machine instruction constitutes the **microroutine**.
    - The microroutines for all instructions in the instruction-set of a computer are stored in a special memory called the **Control Store (CS)**.
    - Control-unit generates control-signals for any instruction by sequentially reading CWs of corresponding microroutine from CS.
    - **μPC** is used to read CWs sequentially from CS. (μPC □ Microprogram Counter).
    - Every time new instruction is loaded into IR, o/p of **Starting Address Generator** is loaded into μPC.
    - Then, μPC is automatically incremented by clock; causing successive microinstructions to be read from CS.
- Hence, control-signals are delivered to various parts of processor in correct sequence.

### Advantages

- It simplifies the design of control unit. Thus it is both, cheaper and less error prone implement. Control functions are implemented in software rather than hardware. The design process is orderly and systematic. More flexible, can be changed to accommodate new system specifications or to correct the design errors quickly and cheaply. Floating point arithmetic can be realized efficiently. Complex function such as floating point arithmetic can be realized efficiently.

### Disadvantages

A microprogrammed control unit is somewhat slower than the hardwired control unit, because it takes some extra hardware cost due to the control unit, because time is required to access the microroutine from CM.

- The flexibility is achieved by using a large memory and its access circuitry.

## Basic Processing Unit & Pipelining

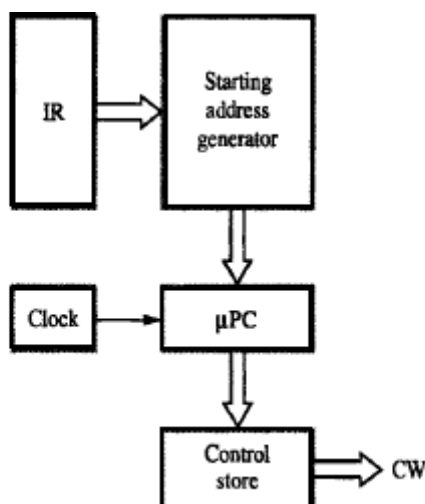


Figure 7.16 Basic organization of a microprogrammed control unit.

Micro - instruction	..	PC <sub>in</sub>	PC <sub>out</sub>	MAR <sub>in</sub>	Read	MDR <sub>out</sub>	IR <sub>in</sub>	Y <sub>in</sub>	Select	Add	Z <sub>in</sub>	Z <sub>out</sub>	R1 <sub>out</sub>	R1 <sub>in</sub>	R3 <sub>out</sub>	WMFC	End	:
1		0	1	1	1	0	0	0	1	1	1	0	0	0	0	0	0	
2		1	0	0	0	0	0	1	0	0	0	1	0	0	0	1	0	
3		0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	

Figure 7.15 An example of microinstructions for Figure 7.6.

### ORGANIZATION OF MICROPROGRAMMED CONTROL UNIT TO SUPPORT CONDITIONAL BRANCHING

#### • Drawback of previous Microprogram control:

➤ It cannot handle the situation when the control unit is required to check the status of the condition codes or external inputs to choose between alternative courses of action.

#### Solution:

➤ Use conditional branch microinstruction.

- In case of conditional branching, microinstructions specify which of the external inputs, condition- codes should be checked as a condition for branching to take place.

- **Starting and Branch Address Generator Block** loads a new address into μPC when a microinstruction instructs it to do so (Figure 7.18).

- To allow implementation of a conditional branch, inputs to this block consist of
  - external inputs and condition-codes &
  - contents of IR.


- μPC is incremented every time a new microinstruction is fetched from microprogram memory except in following situations:

## Basic Processing Unit & Pipelining

- 1) When a new instruction is loaded into IR,  $\mu$ PC is loaded with starting-address of microroutine for that instruction.
- 2) When a Branch microinstruction is encountered and branch condition is satisfied,  $\mu$ PC is loaded with branch-address.
- 3) When an End microinstruction is encountered,  $\mu$ PC is loaded with address of first CW in microroutine for instruction fetch cycle.

Address	Microinstruction
0	$PC_{out}, MAR_{in}, Read, Select4, Add, Z_{in}$
1	$Z_{out}, PC_{in}, Y_{in}, WMFC$
2	$MDR_{out}, IR_{in}$
3	Branch to starting address of appropriate microroutine
25	If $N=0$ , then branch to microinstruction 0
26	Offset-field-of- $IR_{out}, SelectY, Add, Z_{in}$
27	$Z_{out}, PC_{in}, End$

**Figure 7.17** Microroutine for the instruction Branch < 0.

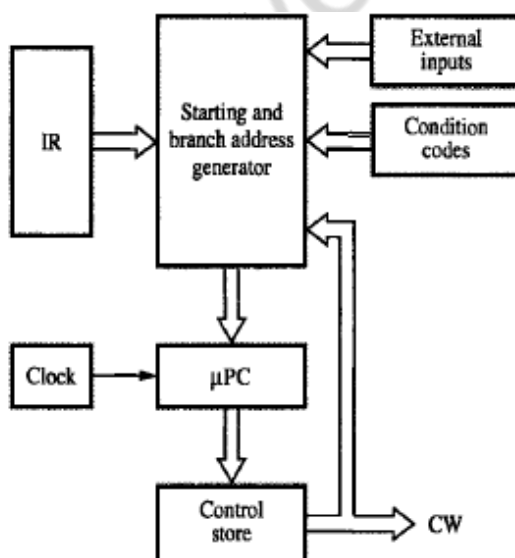

**Figure 7.18** Organization of the control unit to allow conditional branching in the microprogram.



## Basic Processing Unit & Pipelining

### MICROINSTRUCTIONS

• A simple way to structure microinstructions is to assign one bit position to each control-signal required in the CPU.

• There are 42 signals and hence each microinstruction will have 42 bits.

• **Drawbacks of microprogrammed control:**

- 1) Assigning individual bits to each control-signal results in long microinstructions because the number of required signals is usually large.
- 2) Available bit-space is poorly used because only a few bits are set to 1 in any given microinstruction.

• **Solution:** Signals can be grouped because

- 1) Most signals are not needed simultaneously.
- 2) Many signals are mutually exclusive. E.g. only 1 function of ALU can be activated at a time. For ex: Gating signals: IN and OUT signals (Figure 7.19).

Control-signals: Read, Write.

ALU signals: Add, Sub, Mul, Div, Mod.

• Grouping control-signals into fields requires a little more hardware because decoding-circuits must be used to decode bit patterns of each field into individual control-signals.

• **Advantage:** This method results in a smaller control-store (only 20 bits are needed

Microinstruction				
F1	F2	F3	F4	F5
F1 (4 bits)	F2 (3 bits)	F3 (3 bits)	F4 (4 bits)	F5 (2 bits)
0000: No transfer	000: No transfer	000: No transfer	0000: Add	00: No action
0001: PC <sub>out</sub>	001: PC <sub>in</sub>	001: MAR <sub>in</sub>	0001: Sub	01: Read
0010: MDR <sub>out</sub>	010: IR <sub>in</sub>	010: MDR <sub>in</sub>	⋮	10: Write
0011: Z <sub>out</sub>	011: Z <sub>in</sub>	011: TEMP <sub>in</sub>	⋮	
0100: R0 <sub>out</sub>	100: R0 <sub>in</sub>	100: Y <sub>in</sub>	1111: XOR	
0101: R1 <sub>out</sub>	101: R1 <sub>in</sub>		16 ALU functions	
0110: R2 <sub>out</sub>	110: R2 <sub>in</sub>			
0111: R3 <sub>out</sub>	111: R3 <sub>in</sub>			
1010: TEMP <sub>out</sub>				
1011: Offset <sub>out</sub>				
F6	F7	F8	...	
F6 (1 bit)	F7 (1 bit)	F8 (1 bit)		
0: SelectY	0: No action	0: Continue		
1: Select4	1: WMFC	1: End		

Figure 7.19 An example of a partial format for field-encoded microinstructions.

to store the patterns for the 42 signals).

## Basic Processing Unit & Pipelining

### TECHNIQUES OF GROUPING OF CONTROL-SIGNALS

- The grouping of control-signal can be done either by using

- 1) Vertical organization &
- 2) Horizontal organisation.

Vertical Organization	Horizontal Organization
Highly encoded schemes that use compact codes to specify only a small number of control functions in each microinstruction are referred to as a vertical organization.	The minimally encoded scheme in which many resources can be controlled with a single microinstruction is called a horizontal organization.
Slower operating-speeds.	Useful when higher operating-speed is desired.
Short formats.	Long formats.
Limited ability to express parallel microoperations.	Ability to express a high degree of parallelism.
Considerable encoding of the control information.	Little encoding of the control information.

### MICROPROGRAM SEQUENCING

- The task of microprogram sequencing is done by microprogram sequencer.
- Two important factors must be considered while designing the microprogram sequencer:

- 1) The size of the microinstruction &
- 2) The address generation time.

- The size of the microinstruction should be minimum so that the size of control memory required to store microinstructions is also less.
- This reduces the cost of control memory.
- With less address generation time, microinstruction can be executed in less time resulting better throughput.
- During execution of a microprogram the address of the next microinstruction to be executed has 3 sources:

- 1) Determined by instruction register.
- 2) Next sequential address &

## Basic Processing Unit & Pipelining

---

### 3) Branch.

- Microinstructions can be shared using microinstruction branching.

- **Disadvantage of microprogrammed branching:**


- 1) Having a separate microroutine for each machine instruction results in a large total number of microinstructions and a large control-store.
  - 2) Execution time is longer because it takes more time to carry out the required branches.
    - Consider the instruction *Add src,Rdst* ;which adds the source-operand to the contents of Rdst and places the sum in Rdst.
    - Let source-operand can be specified in following addressing modes (Figure 7.20):
- a) Indexed
  - b) Autoincrement
  - c) Autodecrement
  - d) Register indirect &
  - e) Register direct
- Each box in the chart corresponds to a microinstruction that controls the transfers and operations indicated within the box.
  - The microinstruction is located at the address indicated by the octal number (001,002).

## Basic Processing Unit & Pipelining

---

[www.takeiteasyengineers.com](http://www.takeiteasyengineers.com)
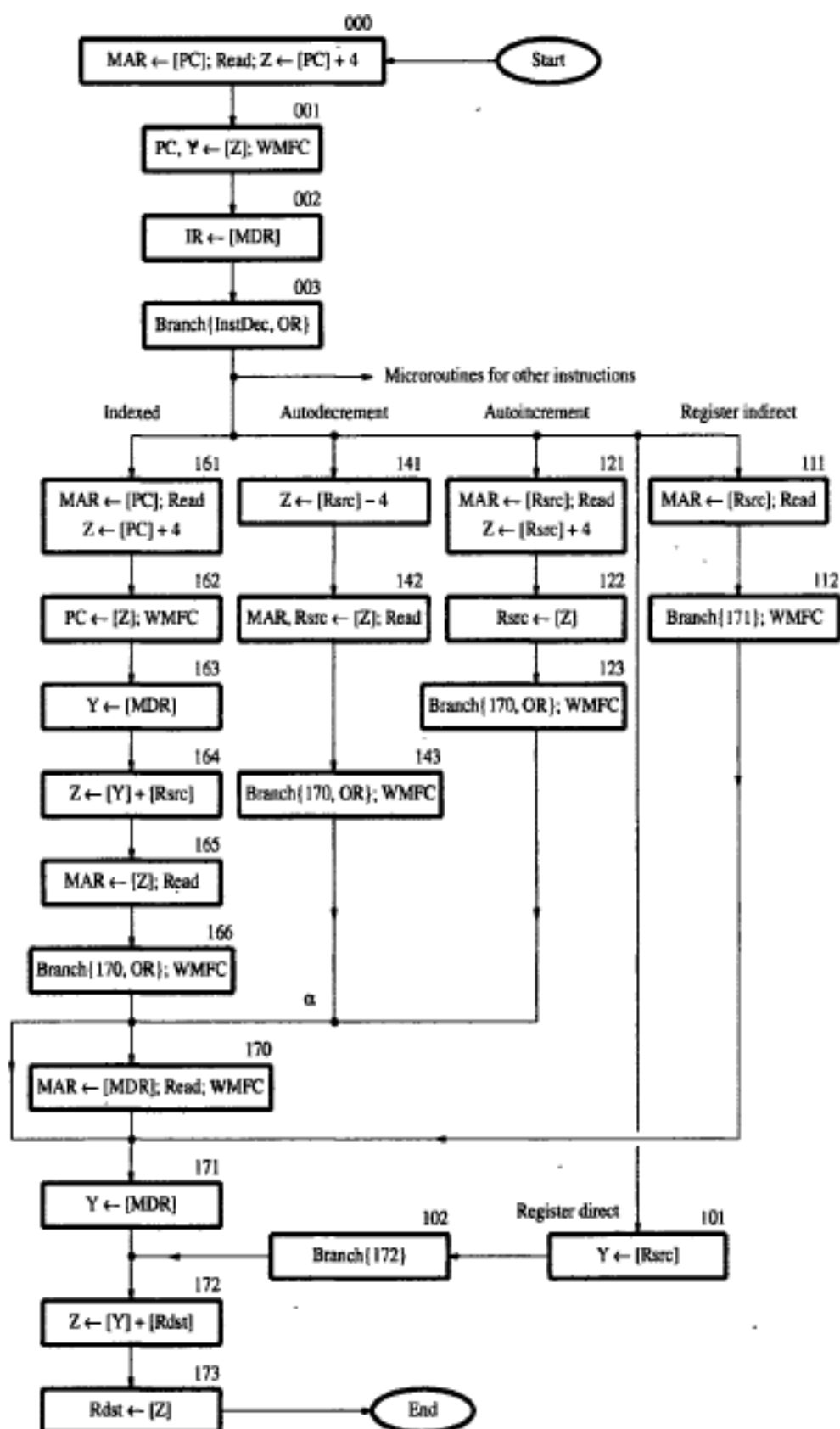
## Basic Processing Unit &amp; Pipelining



## Basic Processing Unit & Pipelining

### BRANCH ADDRESS MODIFICATION USING BIT-ORING

- The branch address is determined by ORing particular bit or bits with the current address of microinstruction.
- **Eg:** If the current address is 170 and branch address is 171 then the branch address can be generated by ORing 01(bit 1), with the current address.
- $\alpha$  Consider the point labeled in the figure. At this point, it is necessary to choose between direct and indirect addressing modes.
- If indirect-mode is specified in the instruction, then the microinstruction in location 170 is performed to fetch the operand from the memory.
- If direct-mode is specified, this fetch must be bypassed by branching immediately to location 171.
- The most efficient way to bypass microinstruction 170 is to have bit-ORing of
  - current address 170 &
  - branch address 171.

### WIDE BRANCH ADDRESSING

- The instruction-decoder (InstDec) generates the starting-address of the microroutine that implements the instruction that has just been loaded into the IR.
- Here, register IR contains the Add instruction, for which the instruction decoder generates the microinstruction address 101. (However, this address cannot be loaded as is into the  $\mu$ PC).
- The source-operand can be specified in any of several addressing-modes. The bit-ORing technique can be used to modify the starting-address generated by the instruction-decoder to reach the appropriate path.


#### Use of WMFC

- WMFC signal is issued at location 112 which causes a branch to the microinstruction in location 171.
- WMFC signal means that the microinstruction may take several clock cycles to complete. If the branch is allowed to happen in the first clock cycle, the microinstruction at location 171 would be fetched and executed prematurely. To avoid this problem, WMFC signal must inhibit any change in the contents of the  $\mu$ PC during the waiting-period.

## Basic Processing Unit & Pipelining
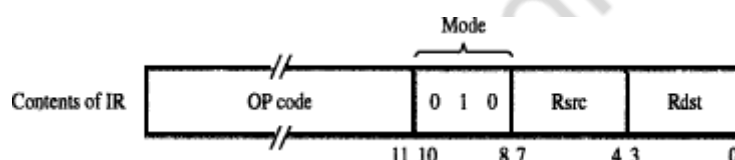
### Detailed Examination of Add (Rsrc)+,Rdst

- Consider *Add (Rsrc)+,Rdst*; which adds Rsrc content to Rdst content, then stores the sum in Rdst and finally increments Rsrc by 4 (i.e. auto-increment mode).
- In bit 10 and 9, bit-patterns 11, 10, 01 and 00 denote indexed, auto-decrement, auto-increment and register modes respectively. For each of these modes, bit 8 is used to specify the indirect version.
- The processor has 16 registers that can be used for addressing purposes; each specified using a 4-bit-code (Figure 7.21).
- There are 2 stages of decoding:
  - 1) The microinstruction field must be decoded to determine that an Rsrc or Rdst register is involved.
  - 2) The decoded output is then used to gate the contents of the Rsrc or Rdst fields



in the IR into a second decoder, which produces the gating-signals for the actual

Address (octal)	Microinstruction
000	$PC_{out}, MAR_{in}, Read, Select4, Add, Z_{in}$
001	$Z_{out}, PC_{in}, Y_{in}, WMFC$
002	$MDR_{out}, IR_{in}$
003	$\mu Branch \{ \mu PC \leftarrow 101 \text{ (from Instruction decoder); } \mu PC_{5,4} \leftarrow [IR_{10,9}]; \mu PC_3 \leftarrow [\overline{IR_{10}}] \cdot [\overline{IR_9}] \cdot [IR_8] \}$
121	$Rsrc_{out}, MAR_{in}, Read, Select4, Add, Z_{in}$
122	$Z_{out}, Rsrc_{in}$
123	$\mu Branch \{ \mu PC \leftarrow 170; \mu PC_0 \leftarrow [\overline{IR_8}] \}, WMFC$
170	$MDR_{out}, MAR_{in}, Read, WMFC$
171	$MDR_{out}, Y_{in}$
172	$Rdst_{out}, SelectY, Add, Z_{in}$
173	$Z_{out}, Rdst_{in}, End$

**Figure 7.21** Microinstruction for Add (Rsrc)+,Rdst.

registers R0 to R15.

## Basic Processing Unit & Pipelining

### MICROINSTRUCTIONS WITH NEXT-ADDRESS FIELDS

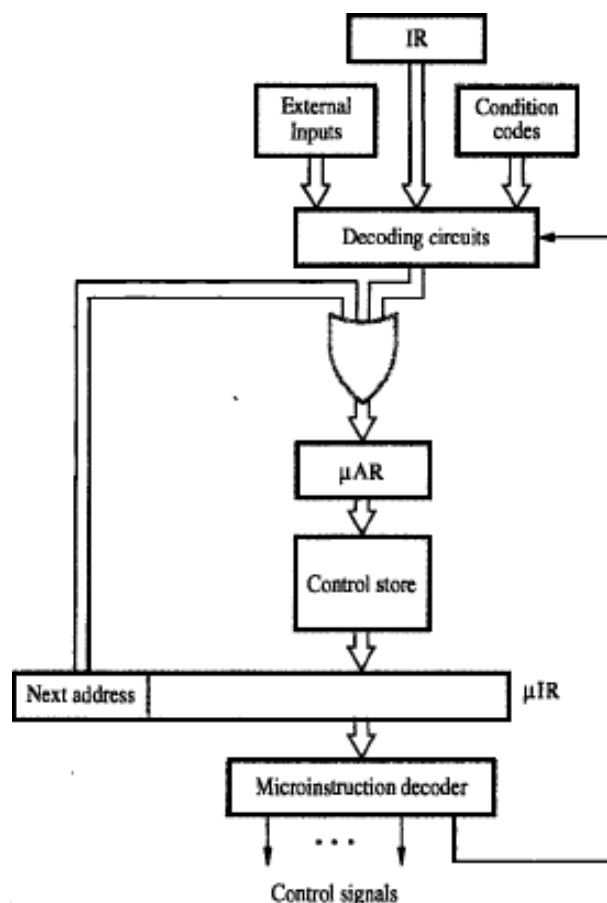


Figure 7.22 Microinstruction-sequencing organization.

#### • Drawback of previous organization:

➤ The microprogram requires several branch microinstructions which perform no useful operation. Thus, they detract from the operating-speed of the computer.

#### Solution:

➤ Include an address-field as a part of every microinstruction to indicate the location of the next microinstruction to be fetched. (Thus, every microinstruction becomes a branch microinstruction).

• The flexibility of this approach comes at the expense of additional bits for the address-field (Fig 7.22).

• **Advantage:** Separate branch microinstructions are virtually eliminated. (Figure 7.23-24).

• **Disadvantage:** Additional bits for the address field (around 1/6).

• There is no need for a counter to keep track of sequential address. Hence,  $\mu PC$  is



## Basic Processing Unit & Pipelining

---

replaced with  $\mu$ AR.

- The next-address bits are fed through the OR gate to the  $\mu$ AR, so that the address can be modified on the basis of the data in the IR, external inputs and condition-codes.
- The decoding circuits generate the starting-address of a given microroutine on the basis of the opcode in the IR. ( $\mu$ AR  $\square$  Microinstruction Address Register).

## Basic Processing Unit &amp; Pipelining

Microinstruction

F0	F1	F2	F3
----	----	----	----

F0 (8 bits)	F1 (3 bits)	F2 (3 bits)	F3 (3 bits)
-------------	-------------	-------------	-------------

Address of next microinstruction	000: No transfer 001: PC <sub>out</sub> 010: MDR <sub>out</sub> 011: Z <sub>out</sub> 100: Rsrc <sub>out</sub> 101: Rdst <sub>out</sub> 110: TEMP <sub>out</sub>	000: No transfer 001: PC <sub>in</sub> 010: IR <sub>in</sub> 011: Z <sub>in</sub> 100: Rsrc <sub>in</sub> 101: Rdst <sub>in</sub>	000: No transfer 001: MAR <sub>in</sub> 010: MDR <sub>in</sub> 011: TEMP <sub>in</sub> 100: Y <sub>in</sub>
----------------------------------	--	--	---

F4	F5	F6	F7
----	----	----	----

F4 (4 bits)	F5 (2 bits)	F6 (1 bit)	F7 (1 bit)
-------------	-------------	------------	------------

0000: Add 0001: Sub ⋮ 1111: XOR	00: No action 01: Read 10: Write	0: SelectY 1: Select4	0: No action 1: WMFC
--	--	--------------------------	-------------------------

F8	F9	F10
----	----	-----

F8 (1 bit)	F9 (1 bit)	F10 (1 bit)
------------	------------	-------------

Octal address	F0	F1	F2	F3	F4	F5	F6	F7	F8	F9	F10
000	00000001	001	011	001	0000	01	1	0	0	0	0
001	00000010	011	001	100	0000	00	0	1	0	0	0
002	00000011	010	010	000	0000	00	0	0	0	0	0
003	00000000	000	000	000	0000	00	0	0	1	1	0
121	01010010	100	011	001	0000	01	1	0	0	0	0
122	01111000	011	100	000	0000	00	0	1	0	0	1
170	01111001	010	000	001	0000	01	0	1	0	0	0
171	01111010	010	000	100	0000	00	0	0	0	0	0
172	01111011	101	011	000	0000	00	0	0	0	0	0
173	00000000	011	101	000	0000	00	0	0	0	0	0

**Figure 7.24** Implementation of the microroutine of Figure 7.21 using a next-microinstruction address field. (See Figure 7.23 for encoded signals.)

## Basic Processing Unit & Pipelining

---

[www.takeiteasyengineers.com](http://www.takeiteasyengineers.com)

## Basic Processing Unit & Pipelining

---

### **PREFETCHING MICROINSTRUCTIONS**

• **Disadvantage of Microprogrammed Control:** Slower operating-speed because of the time it takes to fetch microinstructions from the control-store.

**Solution:** Faster operation is achieved if the next microinstruction is pre-fetched while the current one is being executed.

#### **Emulation**

- The main function of microprogrammed control is to provide a means for simple, flexible and relatively inexpensive execution of machine instruction.
- Its flexibility in using a machine's resources allows diverse classes of instructions to be implemented.
- Suppose we add to the instruction-repository of a given computer M1, an entirely new set of instructions that is in fact the instruction-set of a different computer M2.
- Programs written in the machine language of M2 can be then be run on computer M1 i.e. M1 emulates M2.
- Emulation allows us to replace obsolete equipment with more up-to-date machines.
- If the replacement computer fully emulates the original one, then no software changes have to be made to run existing programs.
- Emulation is easiest when the machines involved have similar architectures.

## Basic Processing Unit & Pipelining

---

**Problem 1:**

Why is the Wait-for-memory-function-completed step needed for reading from or writing to the main memory?

**Solution:**

The WMFC step is needed to synchronize the operation of the processor and the main memory.

**Problem 2:**

For the single bus organization, write the complete control sequence for the instruction: Move (R1), R1

**Solution:**

- PCout, MARin, Read, Select4, Add, Zin
- 2) Zout, PCin, Yin, WMFC
- 3) MDRout, IRin
- 4) R1out, MARin, Read
- 5) MDRinE, WMFC
- 6) MDRout, R2in, End

**Problem 3:****3:**

1)

Write the sequence of control steps required for the single bus organization in each of the following instructions:

- a) Add the immediate number NUM to register R1.
- b) Add the contents of memory-location NUM to register R1.
- c) Add the contents of the memory-location whose address is at memory-location NUM to register R1.

Assume that each instruction consists of two words. The first word specifies the operation and the addressing mode, and the second word contains the number NUM

**Solution:**

## Basic Processing Unit & Pipelining

---

- (a) 1.  $PC_{out}$ ,  $MAR_{in}$ , Read, Select4, Add,  $Z_{in}$   
 2.  $Z_{out}$ ,  $PC_{in}$ ,  $Y_{in}$ , WMFC  
 3.  $MDR_{out}$ ,  $IR_{in}$   
 4.  $PC_{out}$ ,  $MAR_{in}$ , Read, Select4, Add,  $Z_{in}$   
 5.  $Z_{out}$ ,  $PC_{in}$ ,  $Y_{in}$   
 6.  $R1_{out}$ ,  $Y_{in}$ , WMFC  
 7.  $MDR_{out}$ , SelectY, Add,  $Z_{in}$   
 8.  $Z_{out}$ ,  $R1_{in}$ , End
- (b) 1-4. Same as in (a)  
 5.  $Z_{out}$ ,  $PC_{in}$ , WMFC  
 6.  $MDR_{out}$ ,  $MAR_{in}$ , Read  
 7.  $R1_{out}$ ,  $Y_{in}$ , WMFC  
 8.  $MDR_{out}$ , Add,  $Z_{in}$   
 9.  $Z_{out}$ ,  $R1_{in}$ , End
- (c) 1-5. Same as in (b)  
 6.  $MDR_{out}$ ,  $MAR_{in}$ , Read, WMFC  
 7-10. Same as 6-9 in (b)

**Problem 4:**

Show the control steps for the Branch on Negative instruction for a processor with three-bus organization of the data path

**Solution:**

1.  $PC_{out}$ ,  $R=B$ ,  $MAR_{in}$ , Read, IncPC
2. WMFC
3.  $MDR_{outB}$ ,  $R=B$ ,  $IR_{in}$
4.  $PC_{out}$ , Offset field of  $IR_{out}$ , Add, If  $N = 1$  then  $PC_{in}$ , End

## Basic Processing Unit & Pipelining


---

### CONT.): EMBEDDED SYSTEMS & LARGE COMPUTER SYSTEMS

#### MICROWAVE OVEN

- Microwave-oven is one of the examples of embedded-system.
- This appliance is based on **magnetron** power-unit that generates the microwaves used to heat food.
- When turned-on, the magnetron generates its maximum power-output. Lower power-levels can be obtained by turning the magnetron on & off for controlled time-intervals.
- **Cooking Options** include:
  - Manual selection of the power-level and cooking-time.
  - Manual selection of the sequence of different cooking-steps.
  - Automatic melting of food by specifying the weight.
- **Display (or Monitor)** can show following information:
  - Time-of-day clock.
  - Decrementing clock-timer while cooking.
  - Information-messages to the user.
- **I/O Capabilities** include:
  - Input-keys that comprise a 0 to 9 number pad.
  - Function-keys such as Start, Stop, Reset, Power-level etc.
  - Visual output in the form of a LCD.
  - Small speaker that produces the beep-tone.
- **Computational Tasks** executed are:
  - Maintaining the time-of-day clock.
  - Determining the actions needed for the various cooking-options.
  - Generating the control-signals needed to turn on/off devices.
  - Generating display information.

## Basic Processing Unit & Pipelining

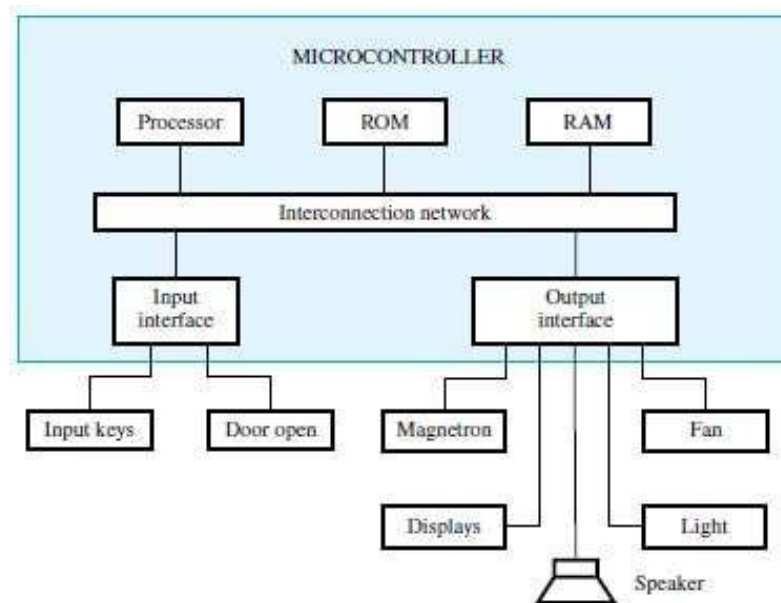

**Figure 10.1** A block diagram of a microwave oven.

- **Non-volatile ROM** is used to store the program required to implement the desired actions. So, the program will not be lost when the power is turned off (Figure 10.1).
  - Most important requirement: The microcontroller must have sufficient I/O capability.

**Parallel I/O Ports** are used for dealing with the external I/O signals.

**Basic I/O Interfaces** are used to connect to the rest of the system.



## Basic Processing Unit & Pipelining


---

[www.takeiteasyengineers.com](http://www.takeiteasyengineers.com)

## Basic Processing Unit & Pipelining

### DIGITAL CAMERA

- Digital Camera is one of the examples of embedded system.
- An array of **Optical Sensors** is used to capture images (Figure 10.2).
- The optical-sensors convert light into electrical charge.

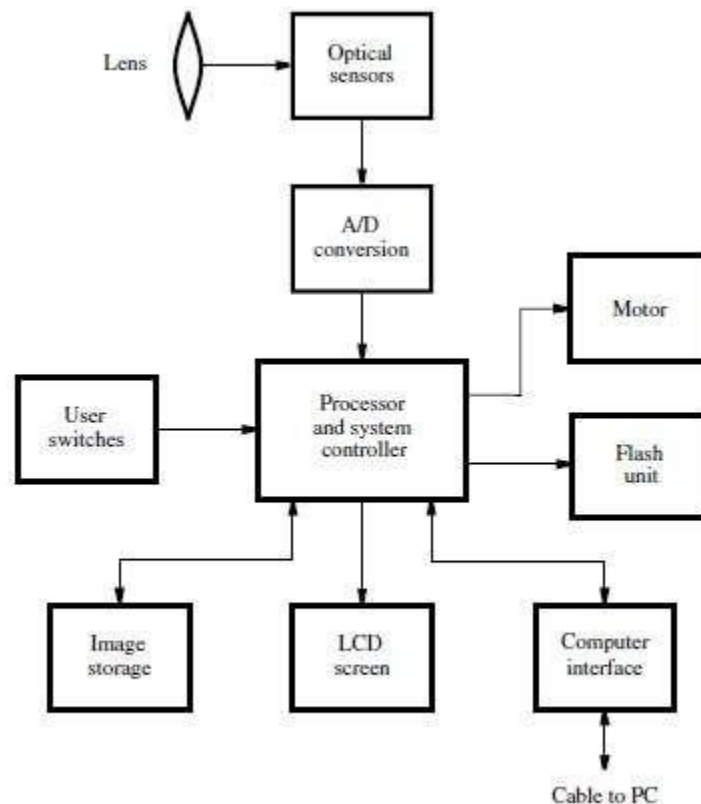

**Figure 10.2** A simplified block diagram of a digital camera.

- Each sensing-element generates a charge that corresponds to one **pixel**. One pixel is one point of a pictorial image.  
The number of pixels determines the quality of pictures that can be recorded & displayed.
- **ADC** is used to convert the charge which is an analog quantity into a digital representation.
- **Processor**
  - manages the operation of the camera.
  - processes the raw image-data obtained from the ADCs to generate images.
- The images are represented in standard-formats, so that they are suitable for use in computers.
- Two standard-formats are:

## Basic Processing Unit & Pipelining

---

1) **TIFF** is used for uncompressed images &

2) **JPEG** is used for compressed images.

- The processed-images are stored in a larger storage-device. For ex: Flash memory cards.

- A captured & processed image can be displayed on a LCD screen of camera.

- The number of saved-images depends on the size of the storage-unit.

- Typically, **USB Cable** is used for transferring the images from camera to the computer.

- **System Controller** generates the signals needed to control the operation of

i) Focusing mechanism and

ii) Flash unit.

(ADC □ Analog-to-digital converter, LCD □ liquid-crystal display)

(TIFF □ Tagged Image File Format, JPEG □ Joint Photographic Experts Group)

## Basic Processing Unit & Pipelining

---

### HOME TELEMETRY (DISPLAY TELEPHONE)

- Home Telemetry is one of the examples of embedded system.
  - The display-telephone has an embedded processor which enables a remote access to other devices in the home.
  - Display telephone can perform following functions:
    - 1) Communicate with a computer-controlled home security-system.
    - 2) Set a desired temperature to be maintained by an air conditioner.
    - 3) Set start-time, cooking-time & temperature for food in the microwave-oven.
    - 4) Read the electricity, gas, and water meters.
  - All of this is easily implementable if each of these devices is controlled by a **microcontroller**.
  - A link (wired or wireless) has to be provided between
    - 1) Device microcontroller &
    - 2) Microprocessor in the telephone.
  - Using signaling from a remote location to observe/control state of device is referred to as **telemetry**.
-

## Basic Processing Unit & Pipelining

### MICROCONTROLLER CHIPS FOR EMBEDDED APPLICATIONS

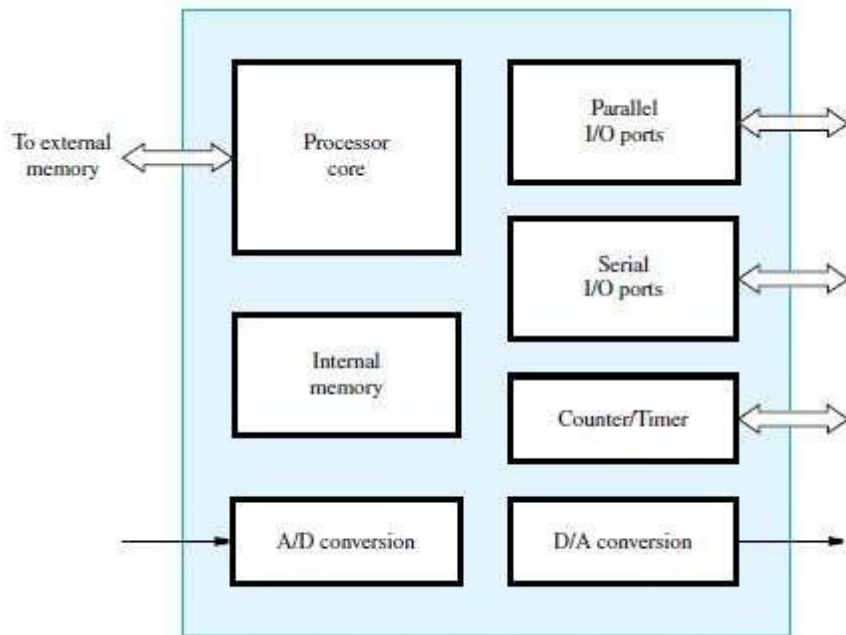


Figure 10.3 A block diagram of a microcontroller.

- **Processor Core** may be a basic version of a commercially available microprocessor (Figure 10.3).
- Well-known popular microprocessor architecture must be chosen. This is because, design of new products is facilitated by
  - numerous CAD tools
  - good examples &
  - large amount of knowledge/experience.
- **Memory-Unit** must be included on the microcontroller-chip.
- The memory-size must be sufficient to satisfy the memory-requirements found in small applications.
- Some memory should be of **RAM** type to hold the data that change during computations. Some memory should be of **Read-Only** type to hold the software. This is because an embedded system usually does not include a magnetic-disk.
- A field-programmable type of ROM storage must be provided to allow cost-effective use. For example: EEPROM and Flash memory.
  - **I/O ports** are provided for both parallel and serial interfaces.
  - **Parallel and Serial Interfaces** allow easy implementation of standard I/O connections.


## Basic Processing Unit & Pipelining

---

- **Timer Circuit** can be used
  - to generate control-signals at programmable time intervals &
  - for event-counting purposes.
- An embedded system may include some **analog devices**.
- **ADC & DAC** are used to convert analog signals into digital representations, and vice versa.


## Basic Processing Unit & Pipelining

### PARALLEL I/O INTERFACE

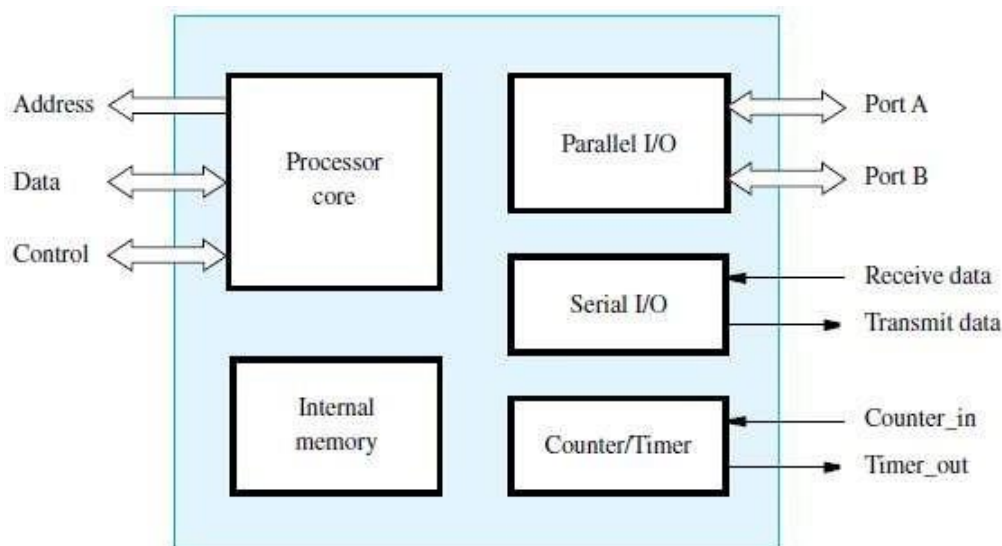

**Figure 10.4** An example microcontroller.

- Each parallel port has an associated 8-bit DDR (Data Direction Register) (Figure 10.4).
- **DDR** can be used to configure individual data lines as either input or output.

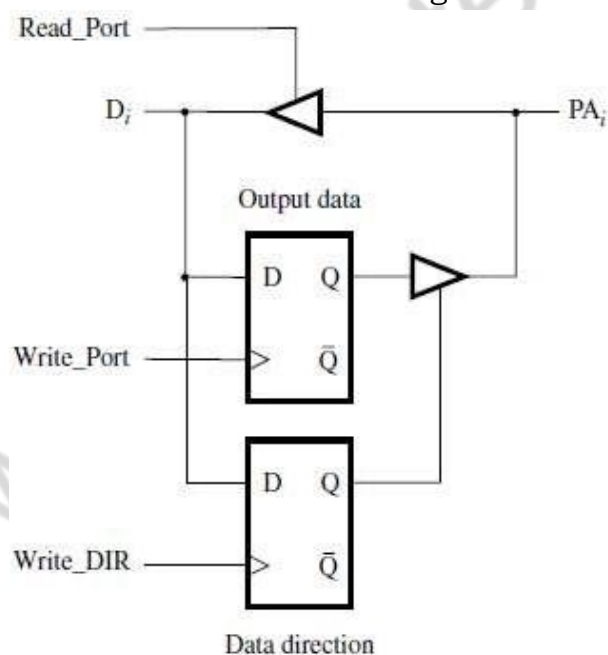

**Figure 10.5** Access to one bit in port A in Figure 10.4.

## Basic Processing Unit & Pipelining

---

- If the data direction flip-flop contains a 0, then Port pin **PAi** is treated as an input (Figure 10.5). If the data direction flip-flop contains a 1, then Port pin PAi is treated as an output.
- Activation of control-signal **Read\_Port**, places the logic value on the port-pin onto the data line Di. Activation of control-signal **Write\_Port**, places value loaded into output data flip-flop onto port-pin.
  - **Addressable Registers** are (Figure 10.6):
    - 1) Input registers (PAIN for port A, PBIN for port B)
    - 2) Output registers (PAOUT for port A, PBOUT for port B)
    - 3) Direction registers (PADIR for port A, PBDIR for port B)
    - 4) Status-register (PSTAT) &
    - 5) Control register (PCONT).



## Basic Processing Unit & Pipelining

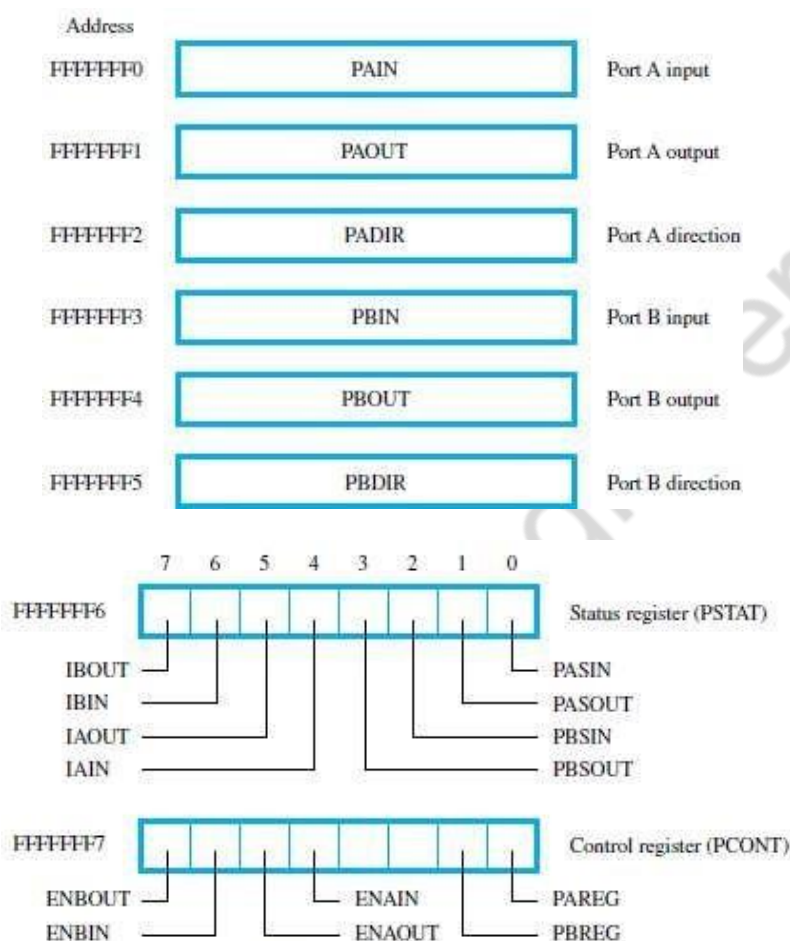


Figure 10.6 Parallel interface registers.

• **Status Register** provides information about the current status of

1) Input registers &

2) Output registers.

• PASIN = 1 □ When there are new data on port A (Figure 10.6).

PASIN = 0 □ When the processor accepts the data by reading the PAIN register.

• The interface uses a separate control line to indicate availability of new data to the connected-device.

• PASOUT = 1 □ When the data in register PAOUT are accepted by the connected-device.

PASOUT = 0 □ When the processor writes data into PAOUT.

• Like PASIN & PAOUT, the flags PBSIN and PBSOUT perform the same function on port B.

• The status register also contains four interrupt flags. They are IAIN, IAOUT, IBIN &

## Basic Processing Unit & Pipelining

---


IBOUT.

- $IAIN = 1$  □ When interrupt is enabled and the corresponding I/O action occurs.
    - The interrupt-enable bits are held in control register PCONT.
    - $ENAIN = 1$  □ when the corresponding interrupt is enabled.
  - For ex: If  $ENAIN=1$  &  $PASIN=1$ , then interrupt flag  $IAIN$  is set to 1 and an interrupt request is raised. Thus,  
 $IAIN = ENAIN * PASIN$ 
    - **Control Registers** is used for controlling data transfers to/from the devices connected to ports A/B.
    - Port A has two control lines:  $CAIN$  and  $CAOUT$ .
    - $CAIN$  and  $CAOUT$  are be used to provide an automatic signaling mechanism b/w
- i) Interface and
- ii) Attached device.
- $PAREG$  and  $PBREG$  are used to select the mode of operation of inputs to ports A and B respectively.
  - If  $PAREG = 1$ ;  
Then, a register is used to store the input data. Otherwise, a direct path from the pins is used.

## Basic Processing Unit & Pipelining

### SERIAL I/O INTERFACE

- The serial interface provides the UART capability to transfer data (Figure 10.7). (UART □ Universal Asynchronous Receiver/Transmitter).
  - Double buffering is
    - used in both the transmit- and receive-paths.
    - needed to handle bursts in I/O transfers correctly.

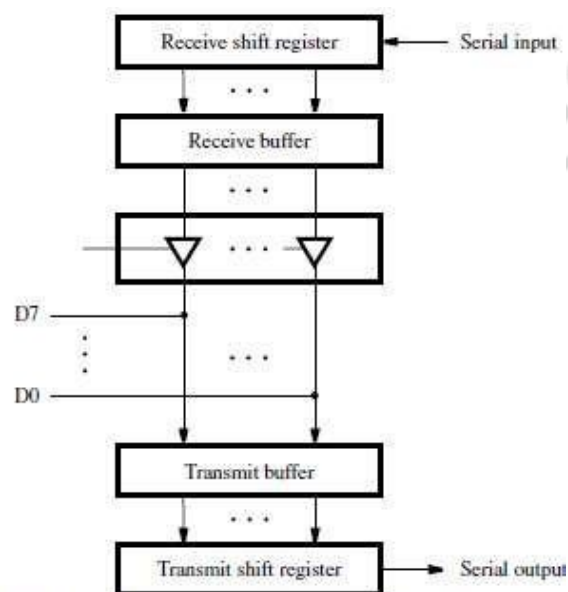


**Figure 10.7** Receive and transmit structure of the serial interface.

• **Addressable Registers** are (Figure 10.8):

- 1) Receive-buffer
- 2) Transmit-buffer
- 3) Status-register (SSTAT)
- 4) Control register (SCONT) &
- 5) Clock-divisor register (DIV).

## Basic Processing Unit & Pipelining

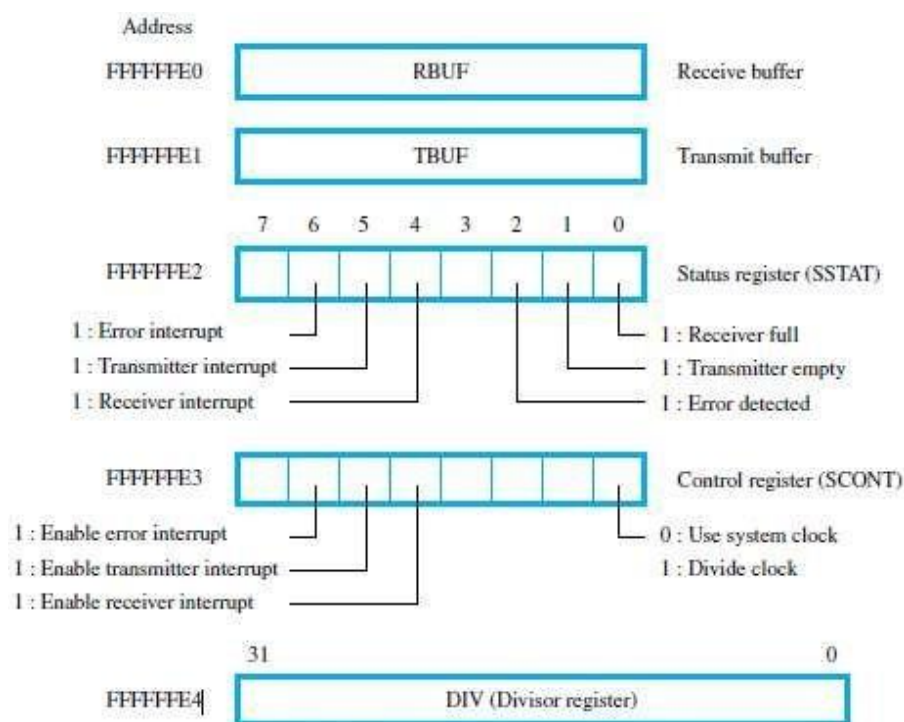

**Figure 10.8** Serial interface registers.


## Basic Processing Unit & Pipelining

- Input data are read from the **Receive-buffer**.  
Output data are loaded into the **Transmit-buffer**.
  - **Status Register** (SSTAT) provides information about the current status of
    - i) Receive-units and
    - ii) Transmit-units.
      - Bit SSTAT0 = 1 □ When there are new data in the receive-buffer.
      - Bit SSTAT0 = 0 □ When the processor accepts the data by reading the receive-buffer.
- SSTAT1 = 1 □ When the data in transmit-buffer are accepted by the connected-device.  
SSTAT1 = 0 □ When the processor writes data into transmit-buffer.  
(SSTAT0 & SSTAT1 similar to SIN & SOUT)
  - SSTAT2 = 1 □ if an error occurs during the receive process.
  - The status-register also contains the interrupt flags.
  - SSTAT4 = 1 □ When the receive-buffer becomes full and the receiver-interrupt is enabled.
  - SSTAT5 = 1 □ When the transmit-buffer becomes empty & the transmitter-interrupt is enabled.
  - **Control Register** (SCONT) is used to hold the interrupt-enable bits.
- If SCONT6-4 = 1.  
Then the corresponding interrupts are enabled. Otherwise, the corresponding interrupts are disabled.
  - Control register also indicates how the transmit clock is generated
- If SCONT0 = 0.  
Then, the transmit clock is the same as the system (processor) clock.  
Otherwise, a lower frequency transmit clock is obtained using a clock-dividing circuit.
  - **Clock-divisor register** (DIV) divides system-clock signal to generate the serial transmission clock.
    - The counter generates a clock signal whose frequency is equal to  
= Frequency of system clock / Contents of DIV register

## Basic Processing Unit & Pipelining

### COUNTER/TIMER

- A 32-bit down-counter-circuit is provided for use as either a counter or a timer.
- Basic operation of the circuit involves
  - loading a starting value into the counter and
  - then decrementing the counter-contents using either
    - i) Internal system clock or
    - ii) External clock signal.
- The circuit can be programmed to raise an interrupt when the counter-contents reach 0.

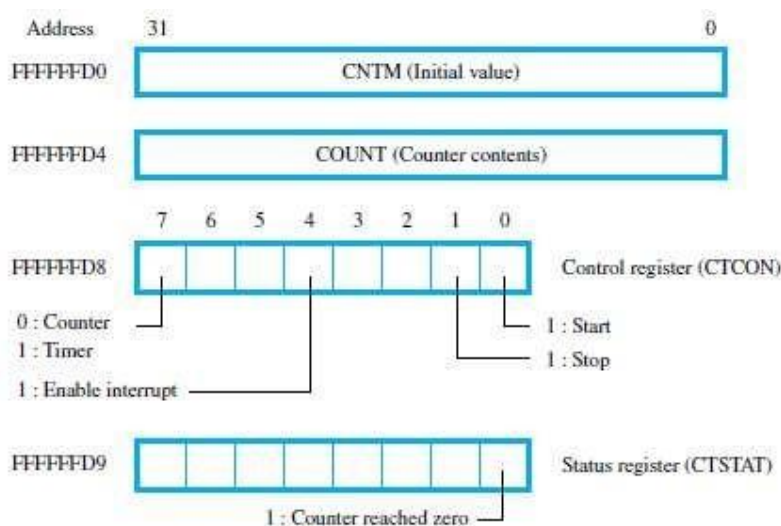

**Figure 10.9** Counter/Timer registers.

- **Counter/Timer Register (CNTM)** can be loaded with an initial value (Figure 10.9).
- The initial value is then transferred into the counter-circuit.
- The current contents of the counter can be read by accessing memory-address FFFFFFFD4.
- **Control Register (CTCON)** is used to specify the operating mode of the counter/timer circuit.
  - The control register provides a mechanism for
    - starting & stopping the counting-process &
    - enabling interrupts when the counter-contents are decremented to 0.
- **Status Register (CTSTAT)** reflects the state of the circuit.
- There are 2 modes: 1) Counter mode 2) Timer mode.

#### Counter Mode

- CTCON7 = 0 □ When the counter mode is selected.
- The starting value is loaded into the counter by writing it into register CNTM.
- The counting-process begins when bit CTCON0 is set to 1 by a program.

## Basic Processing Unit & Pipelining

---

- Once counting starts, bit CTCON0 is automatically cleared to 0.
- The counter is decremented by pulses on the Counter.
- Upon reaching 0, the counter-circuit
  - sets the status flag CTSTAT0 to 1 &
  - raises an interrupt if the corresponding interrupt-enable bit has been set to 1.
- The next clock pulse causes the counter to reload the starting value.
- The starting value is held in register CNTM, and counting continues.
- The counting-process is stopped by setting bit CTCON1 to 1.

### Timer Mode

- CTCON7 = 1 □ When the timer mode is selected.
- This mode can be used to generate periodic interrupts.
- It is also suitable for generating a square-wave signal.
  - The process starts as explained above for the counter mode.
  - As the counter counts down, the value on the output line is held constant.
  - Upon reaching 0, the counter is reloaded automatically with the starting value, and the output signal on the line is inverted.
  - Thus, the period of the output signal is twice the starting counter value multiplied by the period of the controlling clock pulse.
- In the timer mode, the counter is decremented by the system clock.

## Basic Processing Unit & Pipelining

### LE 5(CONT.): THE STRUCTURE OF GENERAL- PURPOSE MULTIPROCESSORS

#### THE STRUCTURE OF GENERAL-PURPOSE MULTIPROCESSORS

##### 1.UMA (Uniform Memory Access) Multiprocessor

- An interconnection-network permits  $n$  processors to access  $k$  memories (Figure 12.2). Thus, any of the processors can access any of the memories.
- The interconnection-network may introduce network-delay between
  - 1) Processor &
  - 2) Memory.
  - A system which has the same network-latency for all accesses from the processors to the memory-modules is called a **UMA Multiprocessor**.
- Although the latency is uniform, it may be large for a network that connects
  - many processors &
  - many memory-modules.
- For better performance, it is desirable to place a memory-module close to each processor.
- **Disadvantage:**
  - Interconnection-networks with very short delays are costly and complex to implement.

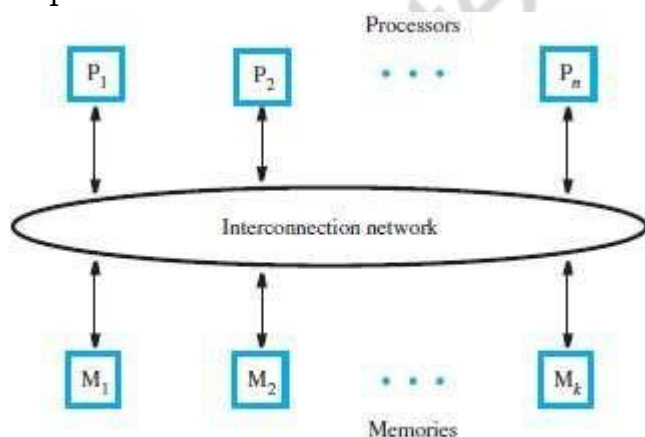


Figure 12.2 A UMA multiprocessor.

##### 2.NUMA (Non-Uniform Memory Access) Multiprocessors

- Memory-modules are attached directly to the processors (Figure 12.3).
- The network-latency is avoided when a processor makes a request to access its local memory.
- However, a request to access a remote-memory-module must pass through the



## Basic Processing Unit & Pipelining

network.


- Because of the difference in latencies for accessing local and remote portions of the shared memory, systems of this type are called **NUMA** multiprocessors.

- **Advantage:**

- A high computation rate is achieved in all processors

- **Disadvantage:**

- The remote accesses take considerably longer than accesses to the local memory.

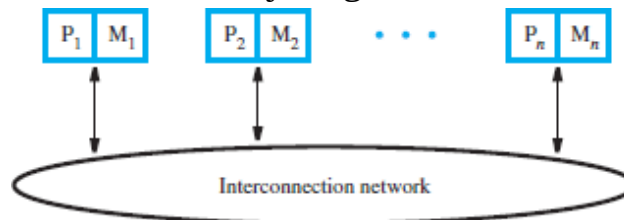

**Figure 12.3** A NUMA multiprocessor.

## Basic Processing Unit & Pipelining

### 3. Distributed Memory Systems

- All memory-modules serve as private memories for processors that are directly connected to them.
- A processor cannot access a remote-memory without the cooperation of the remote- processor.
- This cooperation takes place in the form of messages exchanged by the processors.
- Such systems are often called **Distributed-Memory Systems** (Figure 12.4).

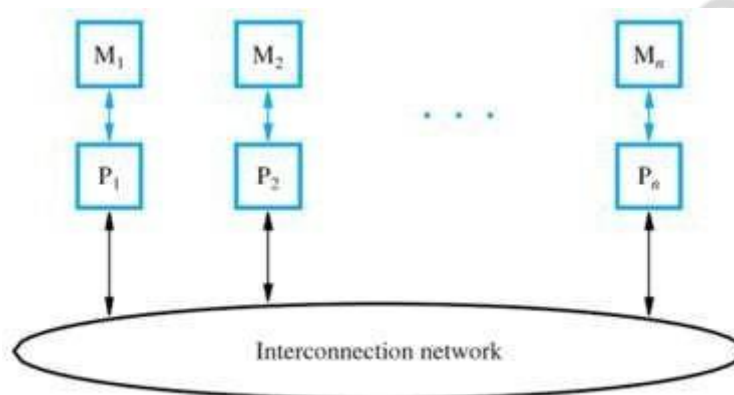


Figure 12.4 A distributed memory system.